

CS1026

Lab #7

30/03/2017



Jakub Slowinski

Student number: 16319781

Design a synchronous sequential circuit called "Div-by-3"

JK flip-flop truth table:

J	K	clock	Q
0	0	1	Q0(no change)
1	0	1	1
0	1	1	0
1	1	1	Q'0(toggles)

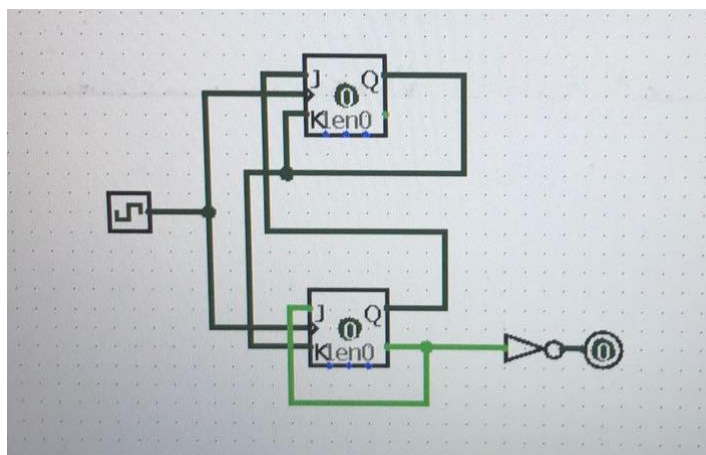 

This divides a system clock frequency by 3.